

WE4A-2

Superconducting Non-reciprocal Bandpass Filter Based on Spatio- Temporal Inductance Modulation

Y. Zhuang*, C. Gaikwad*, D. Kowsari*, E.
Henriksen, K. Murch, and A. Nagulu



*Equal Contribution

Washington University in St. Louis


- Introduction to Quantum Computing Systems
- Superconducting Non-Reciprocal Bandpass Filter Concept
- Simulation Results
- Measurement Setup and Results
- Conclusion

- **Introduction to Quantum Computing Systems**
- **Superconducting Non-Reciprocal Bandpass Filter Concept**
- **Simulation Results**
- **Measurement Setup and Results**
- **Conclusion**

Transmon Qubits Operation

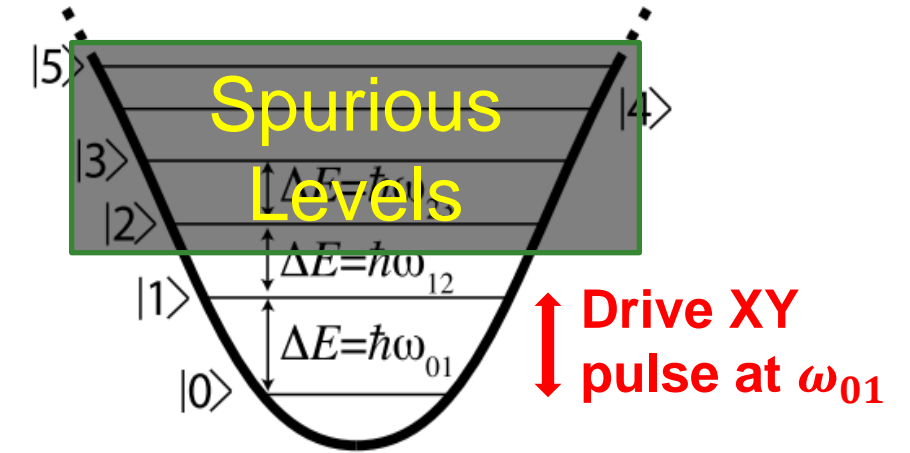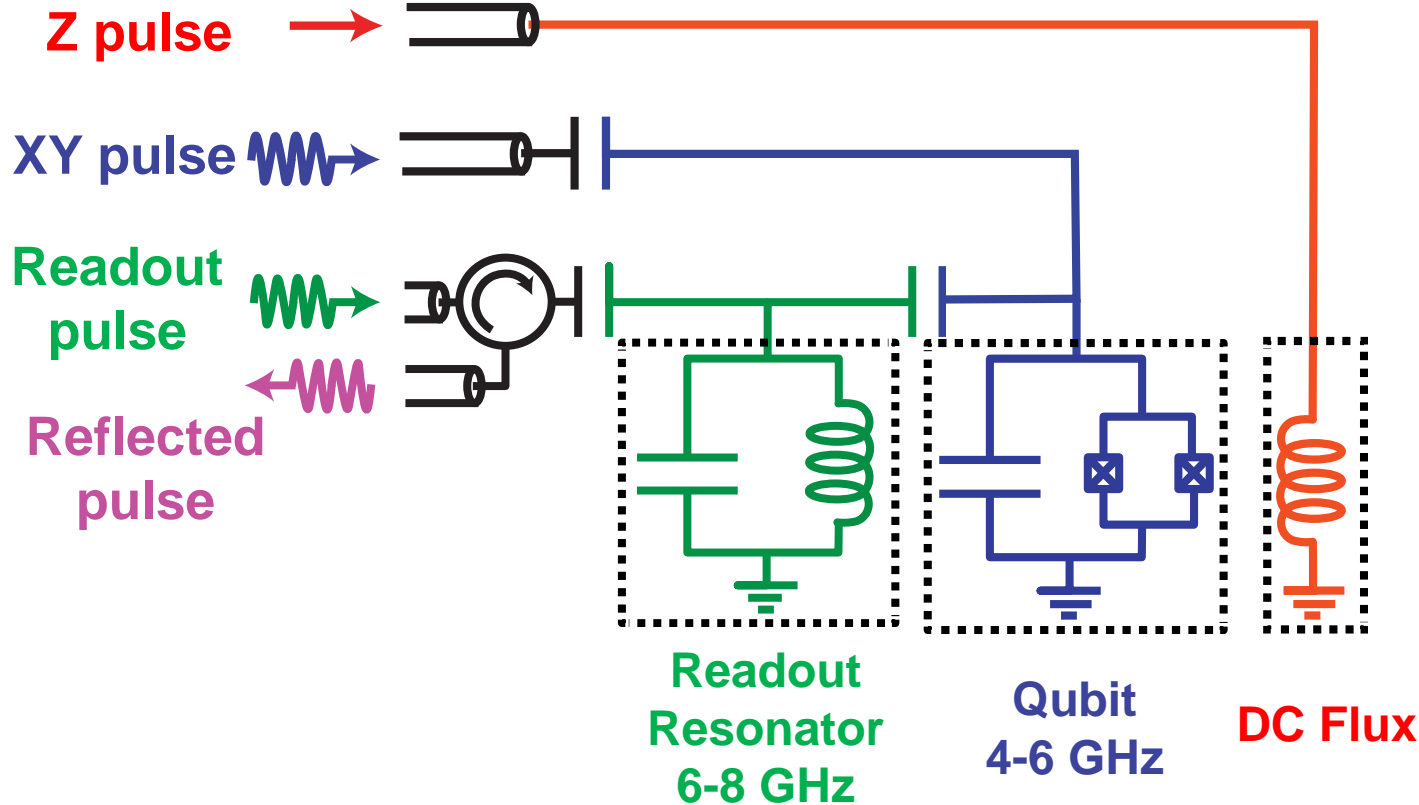


Dispersive Readout

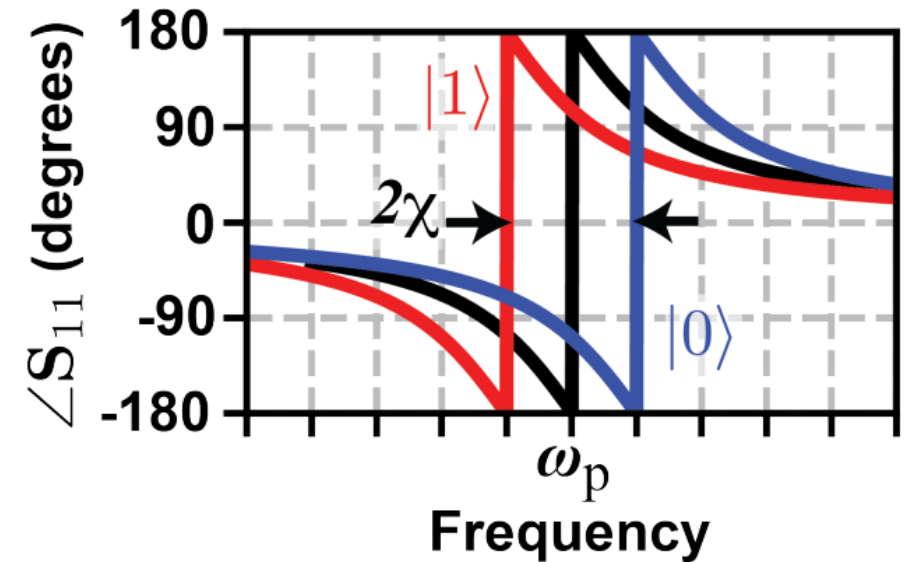


- XY pulse realized qubit gates
- Z pulse change the phase of the state
- Reflectometry based readout measures shift in the readout resonator frequency

Google's Sycamore Quantum Computer

Internals of IBM's Quantum Computer

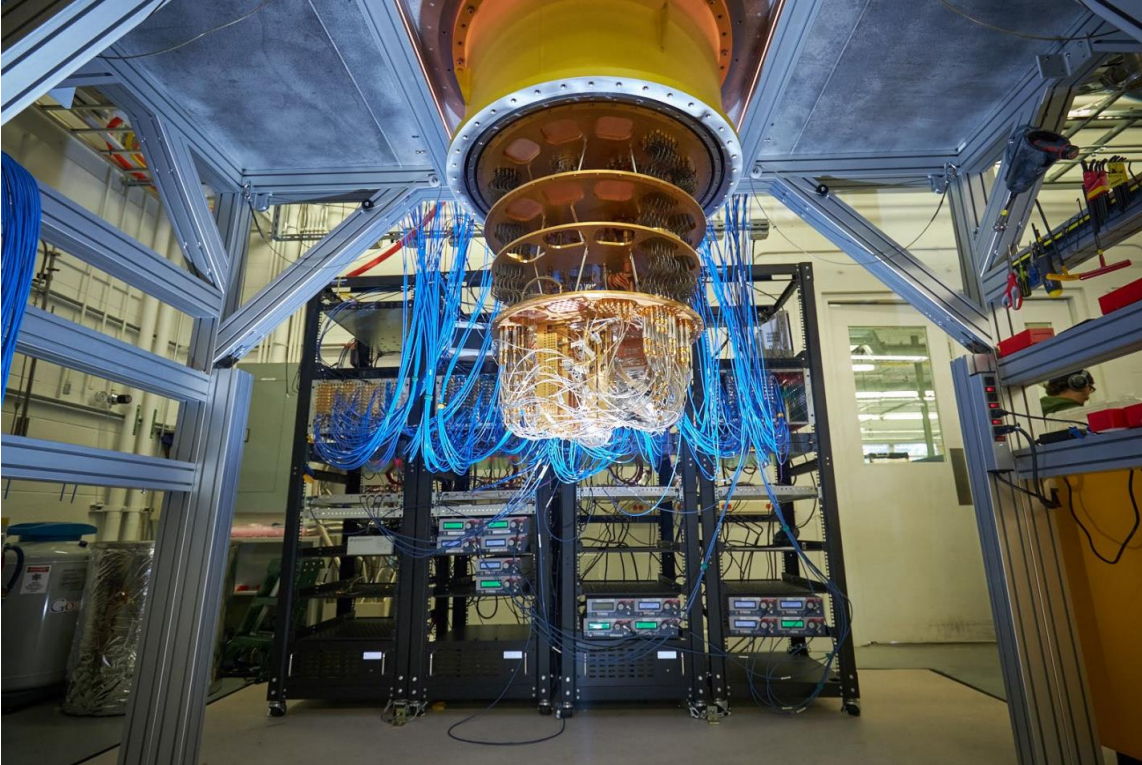

[J. Bardin, ISSCC 2023]

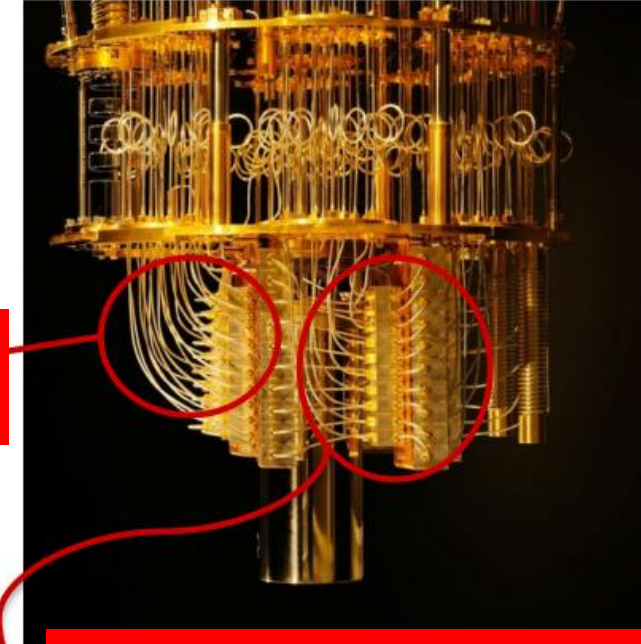


**Cryo Flex
Lines**

**Amplifiers, Attenuators
and Isolators**

[D. Frank, ISSCC 2023]

Currently room temperature equipment, off-the-shelf amplifiers, attenuators and non-reciprocal devices are used for qubit control and readout


Qubit Control & Readout

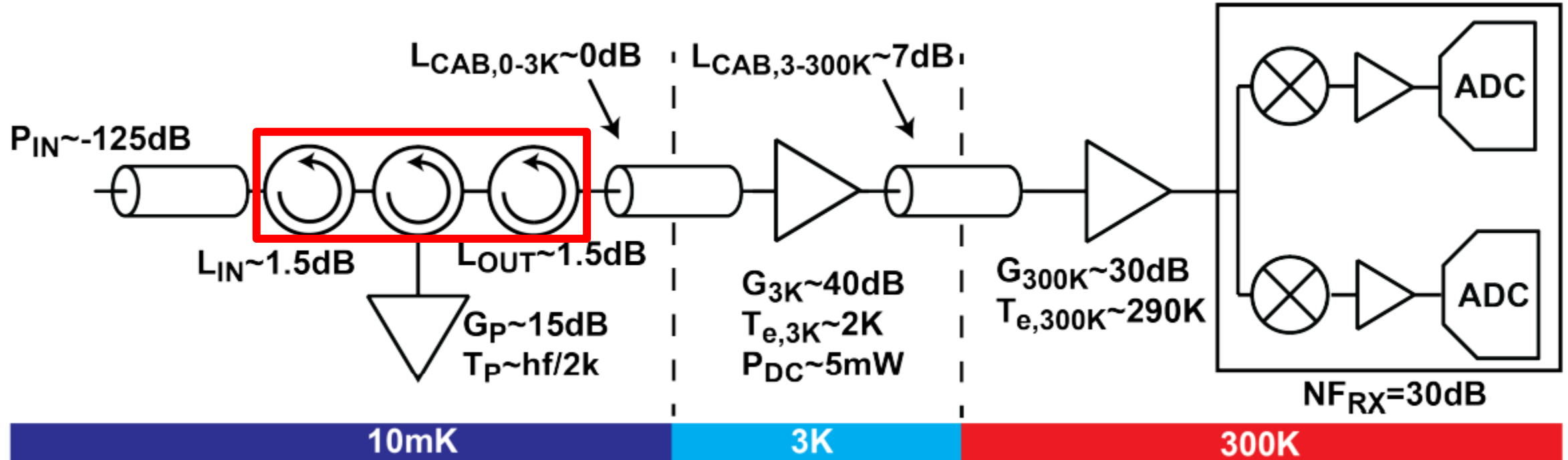

[J. Bardin, ISSCC 2023]

- Fully-Integrated CMOS and superconducting control and readout is scalable, reliable and cost effective
- Isolation is required to protect the qubit from the back reflections

Comparison With Ferrite Isolator

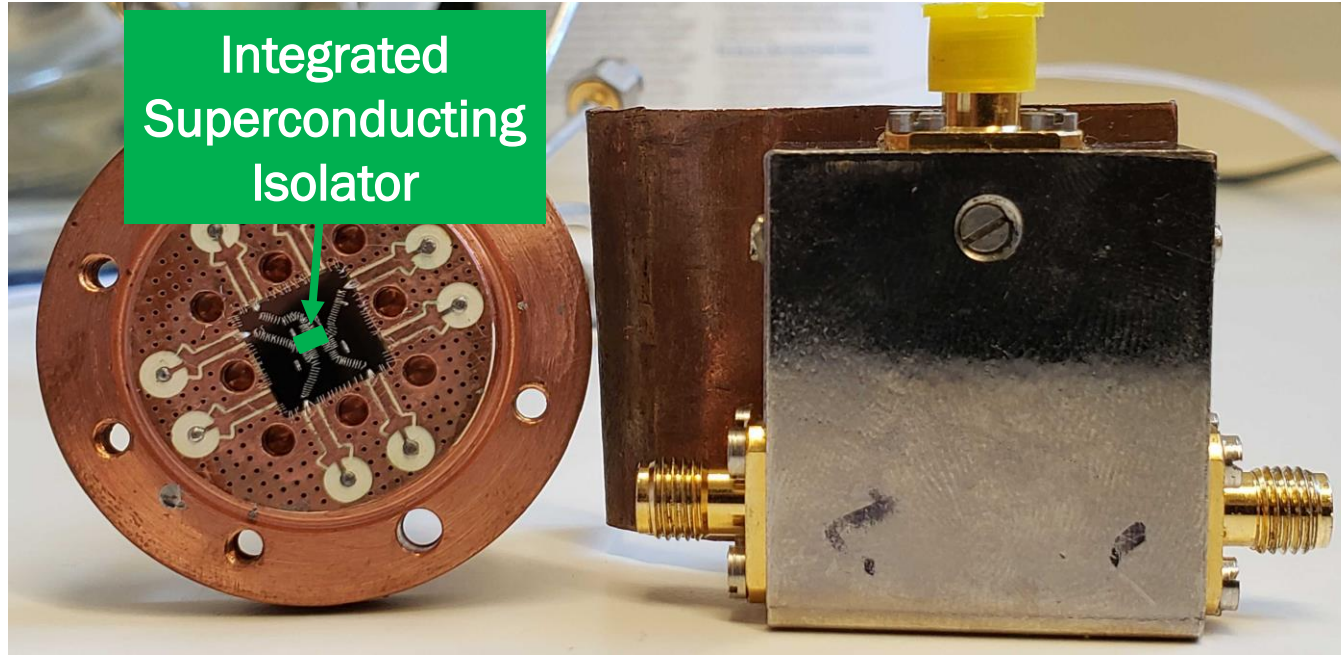


1st Gen. WashU's Isolator
1 × 2 × 0.3 mm
(1 day of a first year Ph.D. student)/ piece

Ferrite Isolator
22.3 × 24.6 × 10.2 mm
(3K\$ – 5K\$)/piece
Source: LNF



- Commercial ferrite circulators/isolators can create undesirable interference due to their strong magnetic bias
- Parametrically modulated isolators does not require strong magnetic bias, 100-1000x compact, and can be fabricated in academic labs at a fraction of cost

- Introduction to Quantum Computing Systems
- **Superconducting Non-Reciprocal Bandpass Filter Concept**
- Simulation Results
- Measurement Setup and Results
- Conclusion



Non-Reciprocal Bandpass Filters

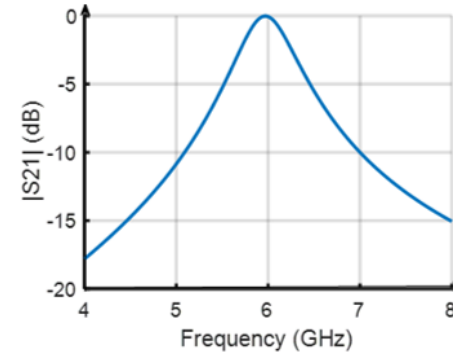

First order Bandpass filter

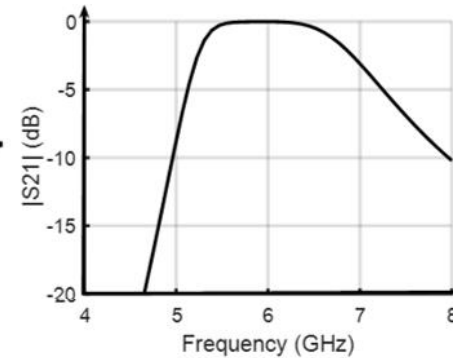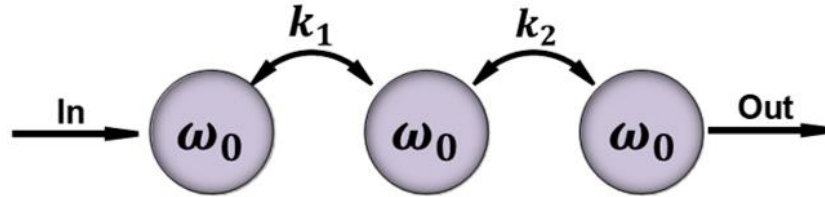


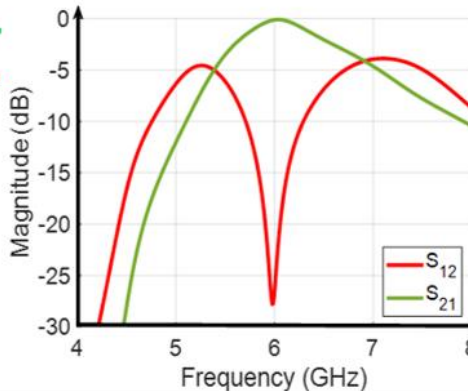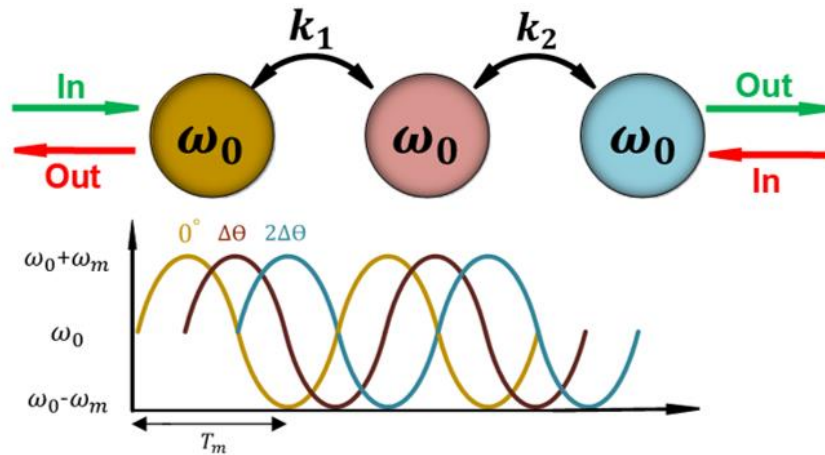Third order Bandpass filter without modulation




Third order Bandpass filter with modulation


Non-Reciprocal Bandpass Filters

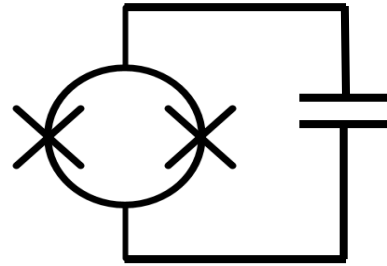

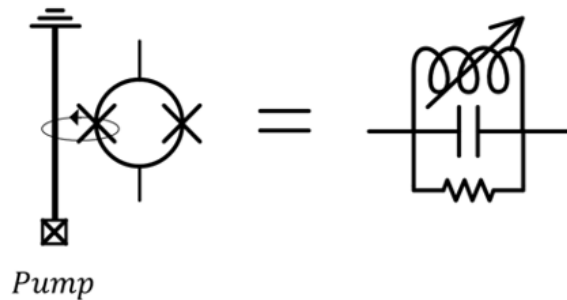- $I_{sig} \ll I_c$
- Increasing I_c require larger capacitor
- Narrow band performance



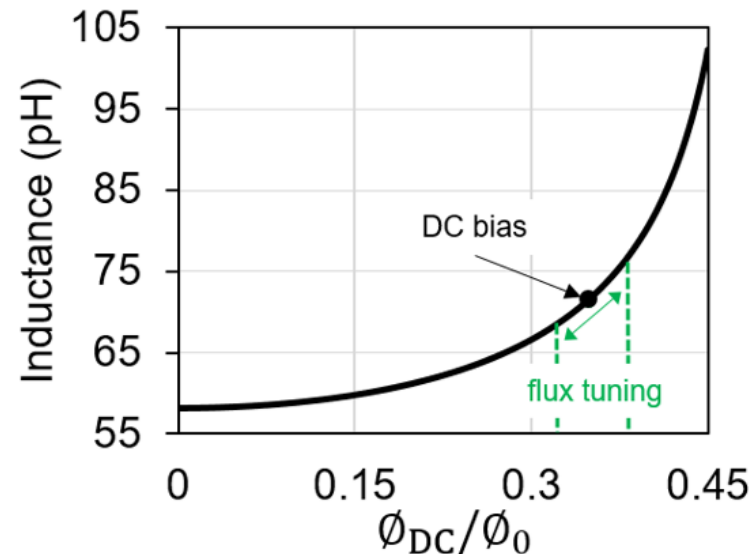
$$L_{SQUID} = \frac{\Phi_0}{4\pi I_c \cos(\frac{\pi\Phi}{\Phi_0})}$$




- SQUID is biased around 0.35 flux quanta


Non-Reciprocal Bandpass Filters

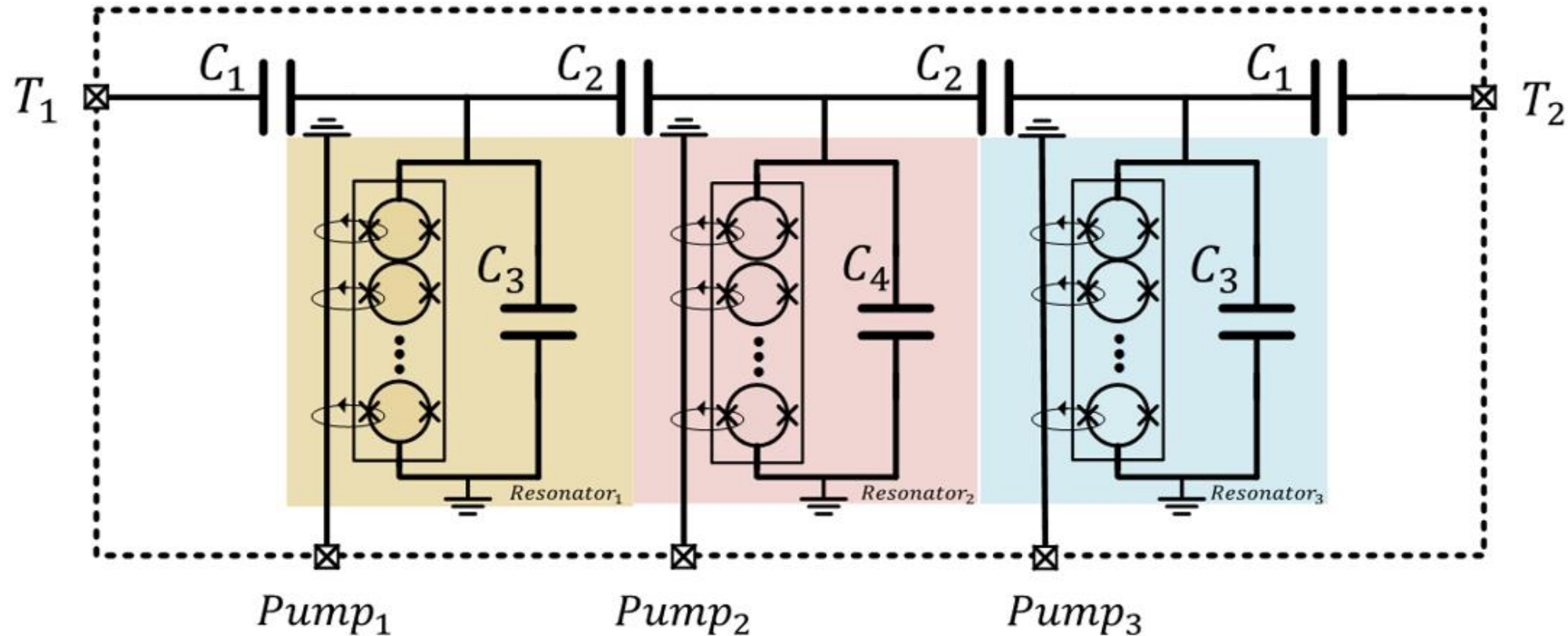

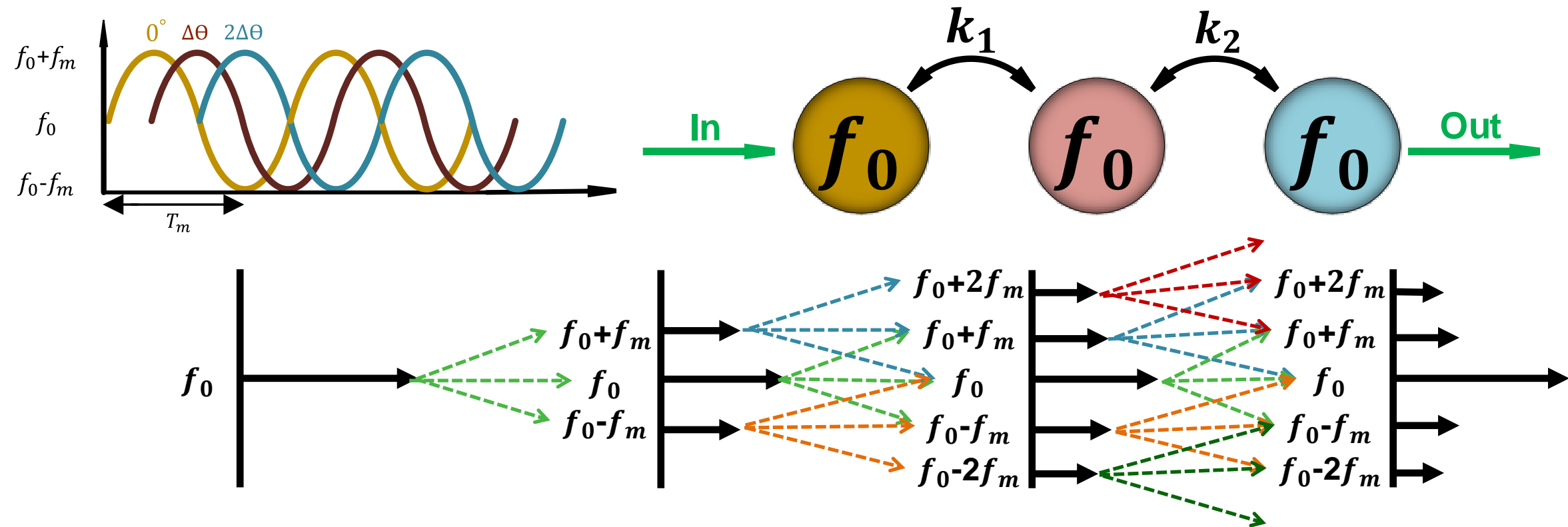- Stacked SQUID structure increases inductance
- Improves power handling
- Support wideband transmission



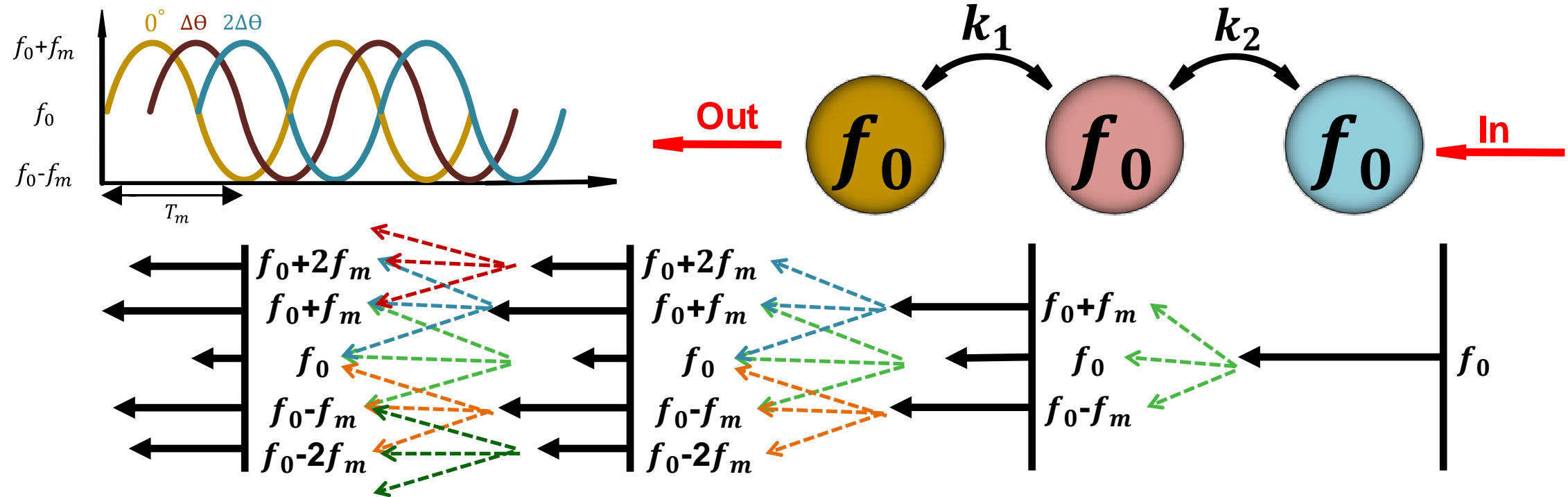
- By choosing proper $\Delta\theta$, IM frequency signal converted back to signal frequency and add up constructively.




- By choosing proper $\Delta\theta$, IM frequency signal converted back to signal frequency and add up destructively.

Comparison


2nd order

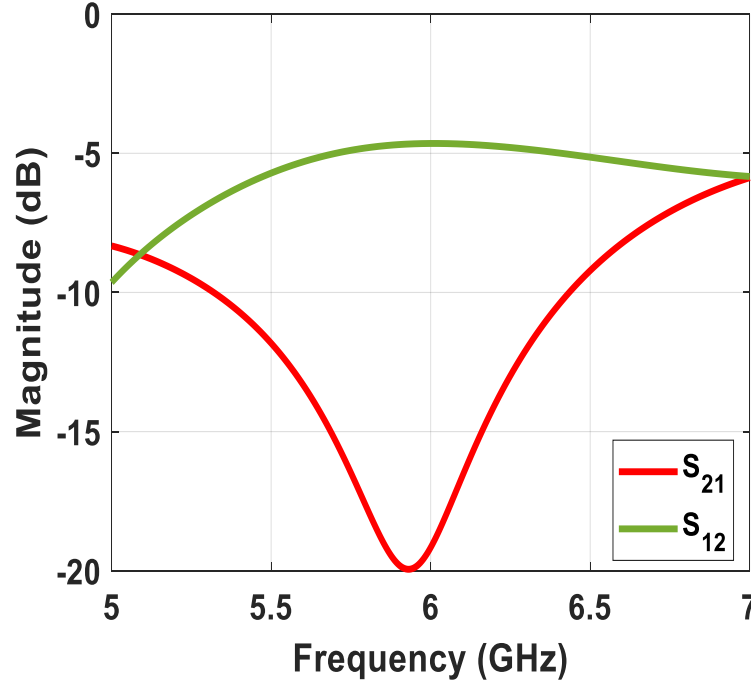

3rd order

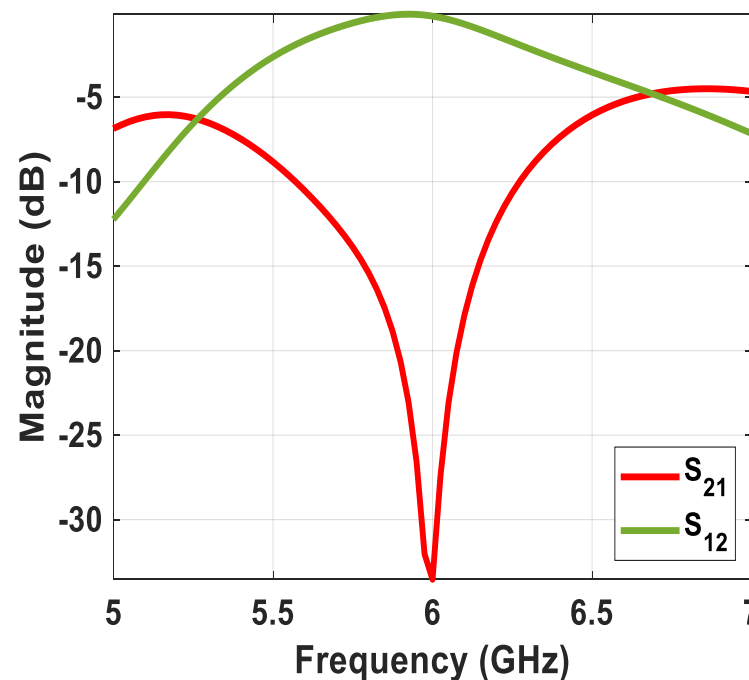


4th order

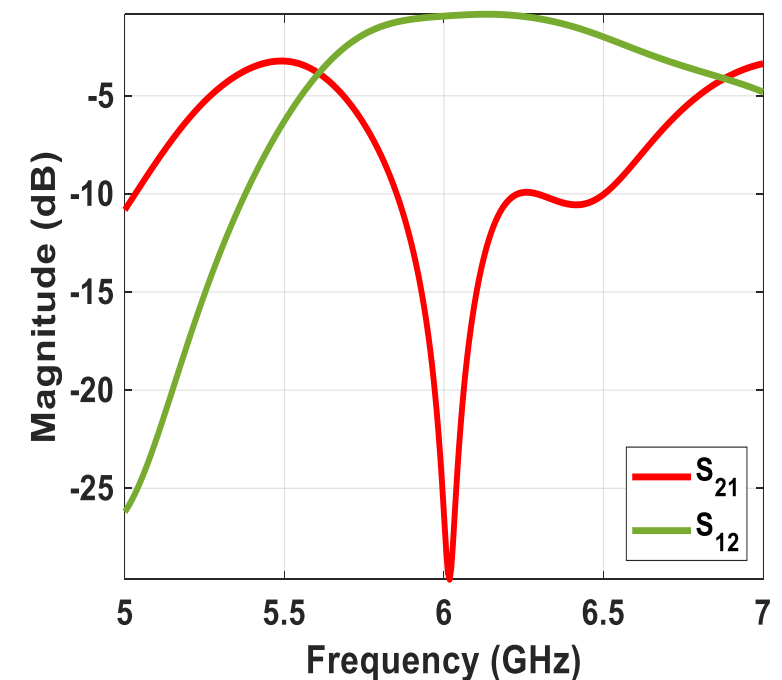


- 2nd order results in high isolation but with high insertion loss
- 3rd order results in high isolation with near-zero insertion loss
- 4th order also has good performance but require larger area

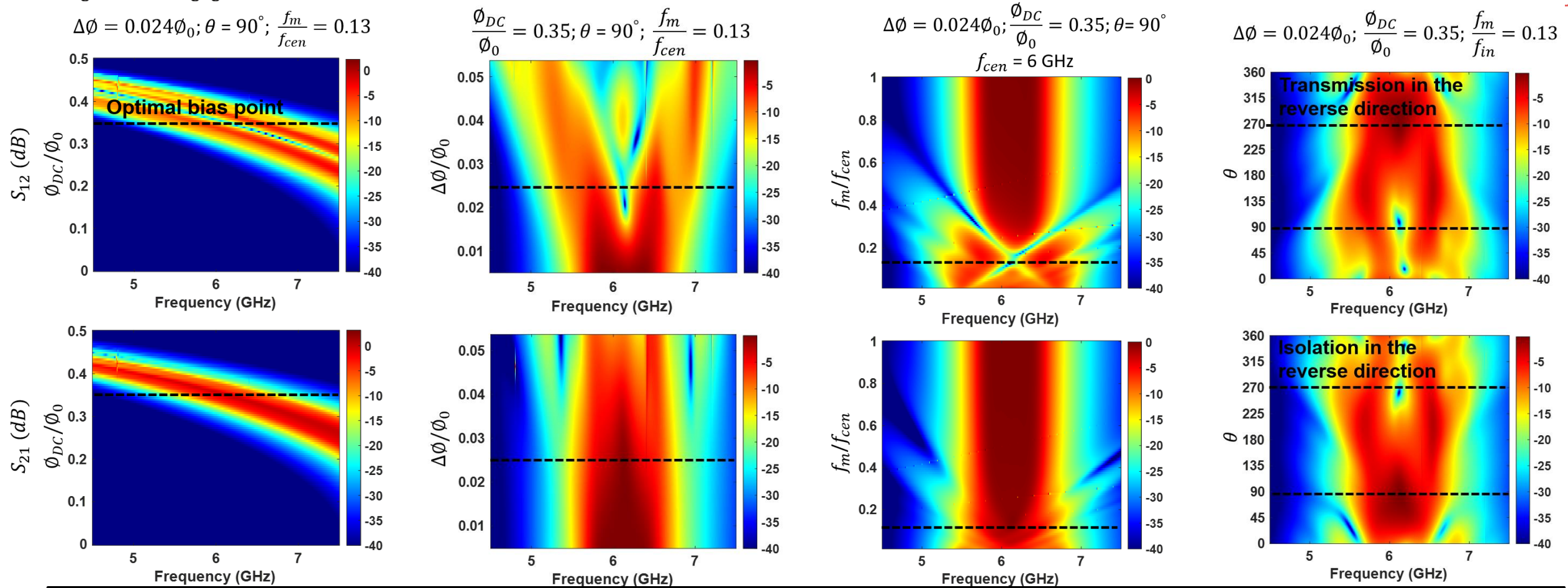- Introduction to Quantum Computing Systems
- Superconducting Non-Reciprocal Bandpass Filter Concept
- **Simulation Results**
- Measurement Setup and Results
- Conclusion



- Modulation parameters: ϕ_{DC} (DC Flux), $\Delta\phi$ (Mod. Amp.), f_m (Mod. Freq.), and θ (phase staggering)
- Optimal modulation parameters are determined through extensive study


S Parameter

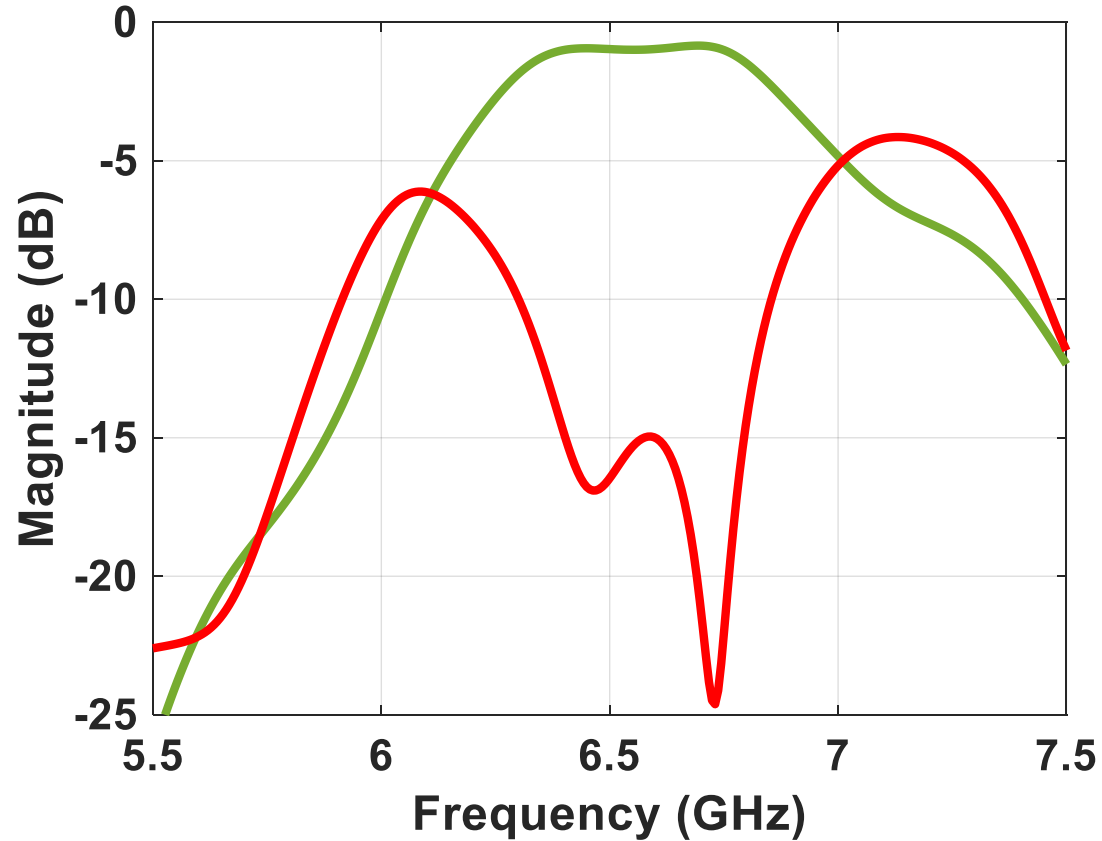

- $\varphi_{DC} = 0.4$ Flux Quanta
- $\Delta\varphi = 0.025$
- $f_m = 770$ MHz
- $\Delta\theta = 124$ degree

- Center frequency at 5.6 GHz
- Insertion loss = 1dB
- Isolation > 20dB across 350 MHz


S Parameter

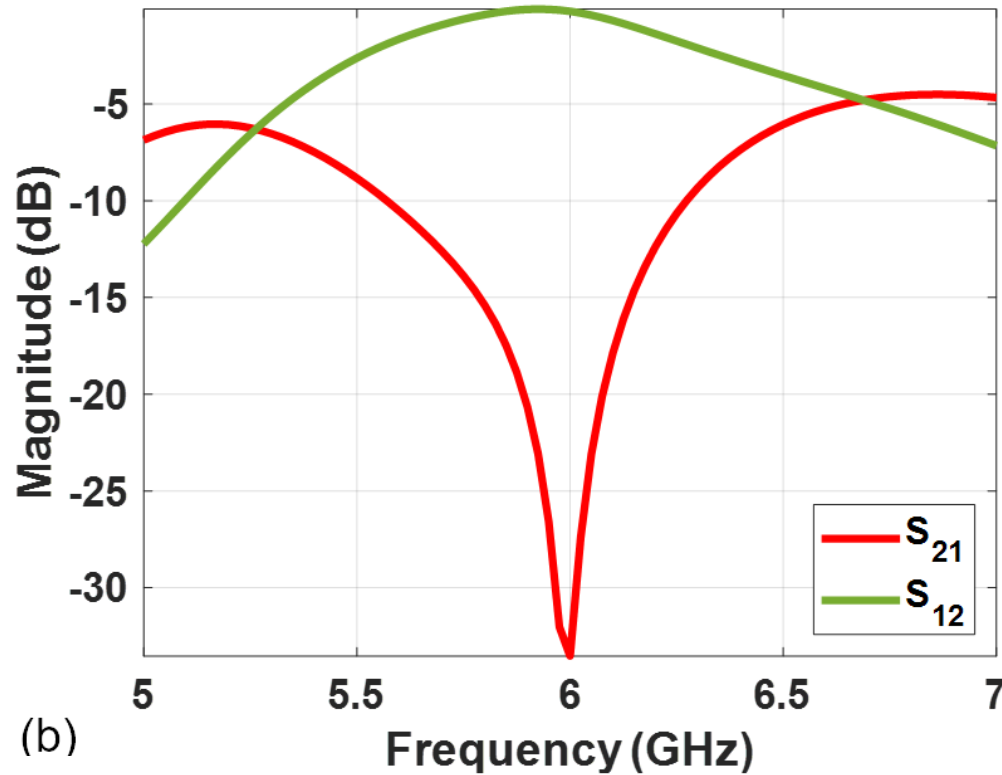


- $\varphi_{DC} = 0.35$ Flux Quanta
- $\Delta\varphi = 0.025$
- $f_m = 700$ MHz
- $\Delta\theta = 90$ degree

- Center frequency at 5.8 GHz
- Insertion loss < 0.5 dB
- Isolation > 15 dB across 200 MHz

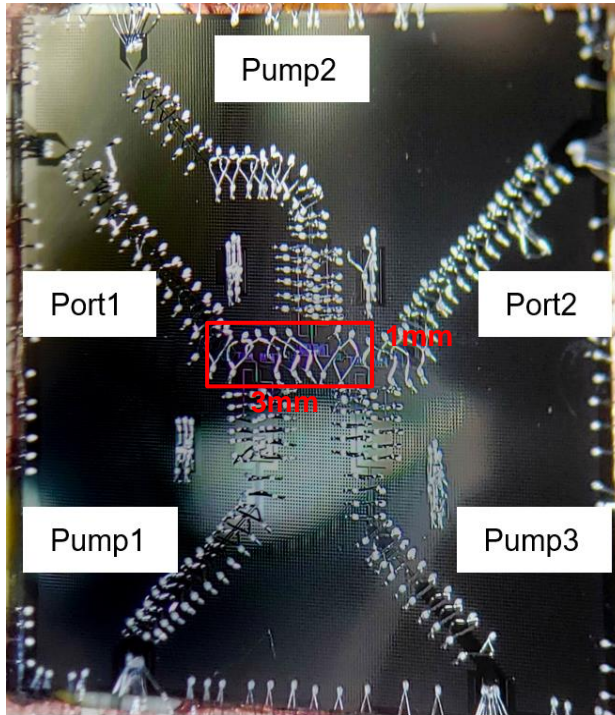
- Introduction to Quantum Computing Systems
- Superconducting Non-Reciprocal Bandpass Filter Concept
- Simulation Results
- **Measurement Setup and Results**
- Conclusion



Chip photo


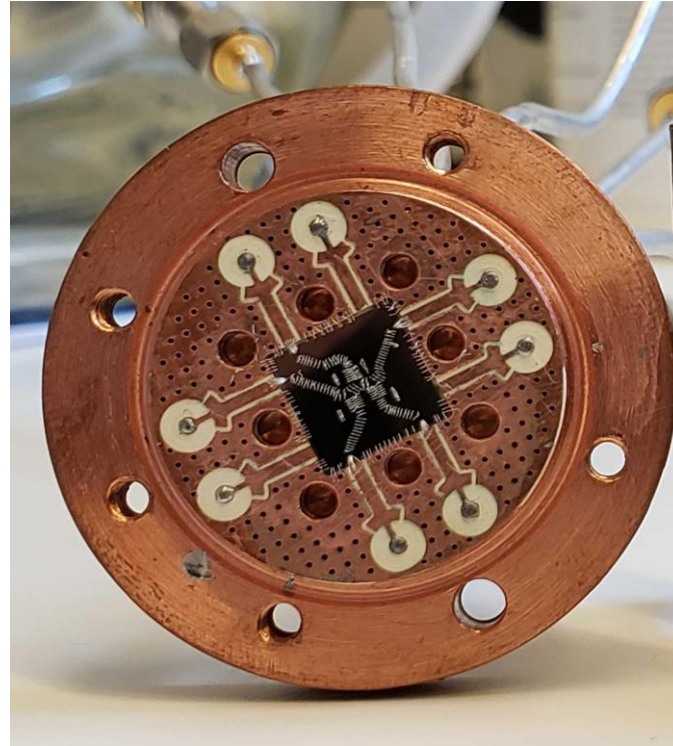


Copper package

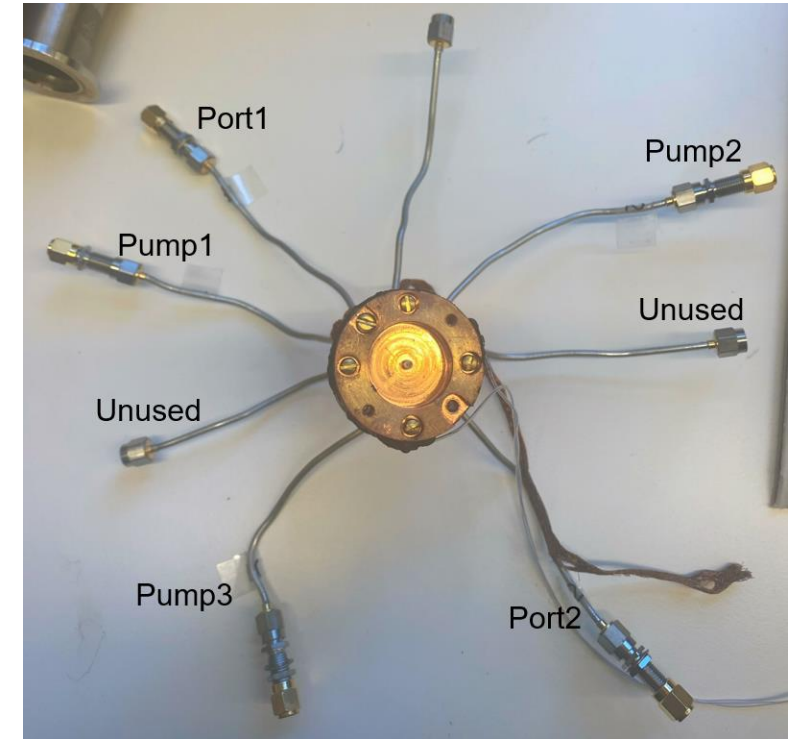

- Chip occupy an area of 3mm x 1mm
- Chip is placed in a copper package with eight ports


Cryogenic Measurement Setup

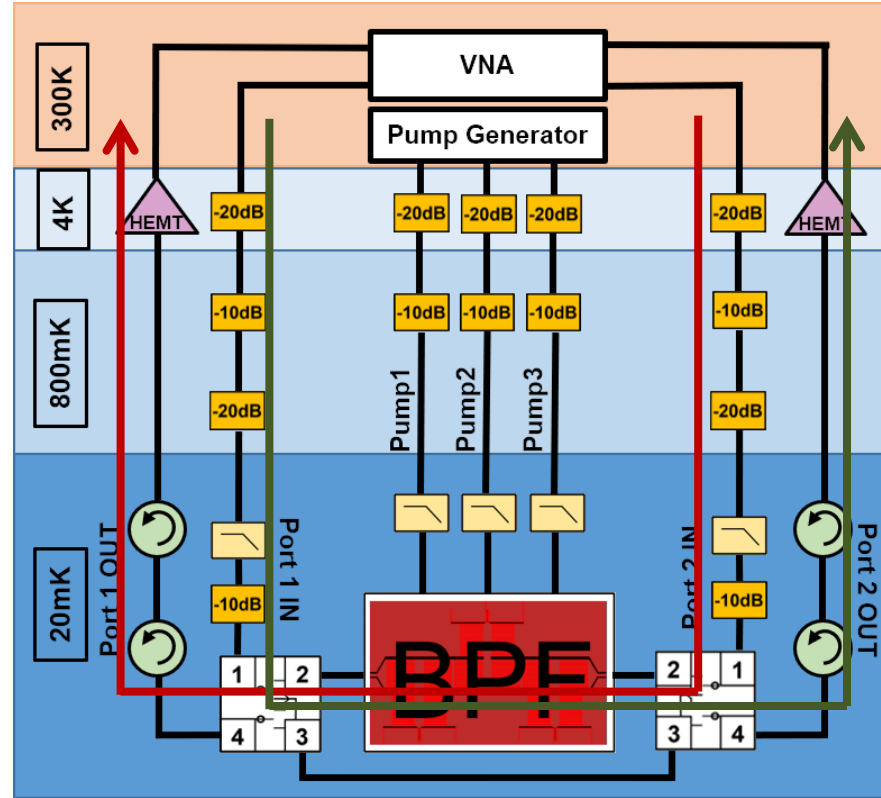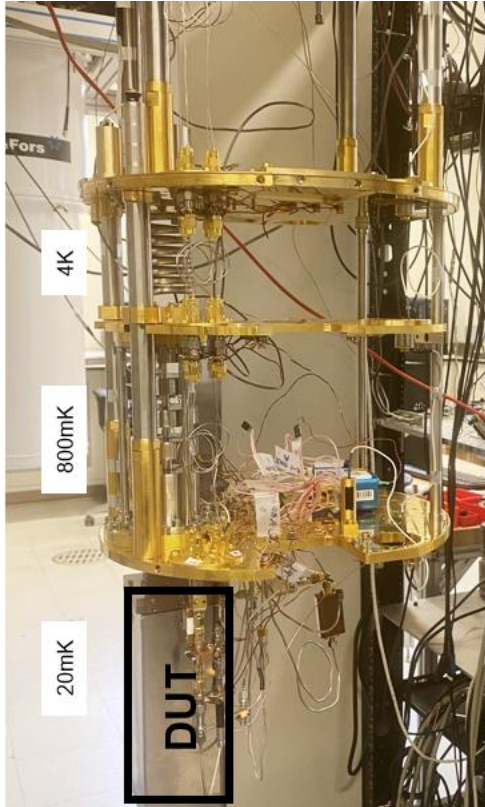




Forward Transmission

Reverse Transmission

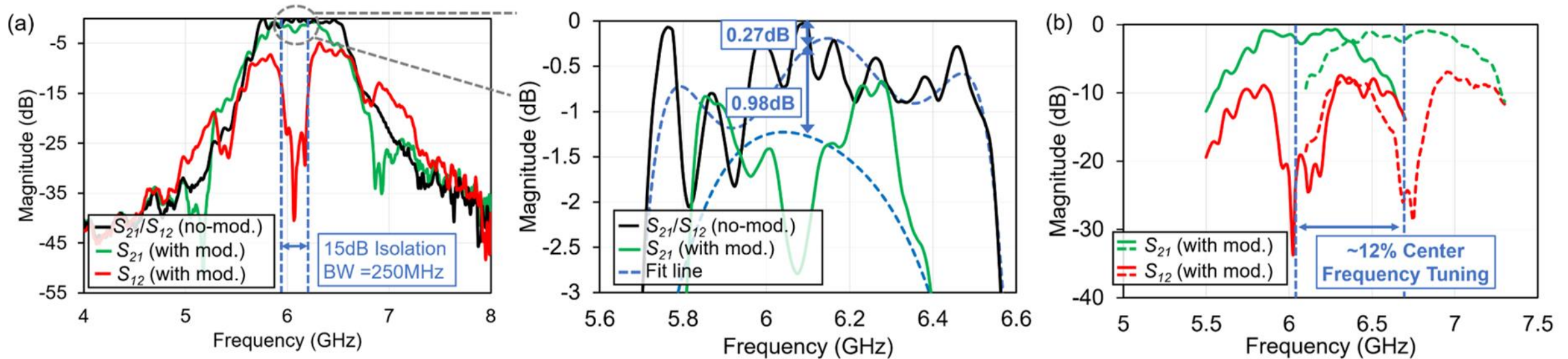- NR-BPF is interfaced with room temperature VNA through cryogenic drive and readout path
- Muxing switches are used to measure the forward and reverse transmissions
- A through line is used to gain-calibrate the drive and readout paths



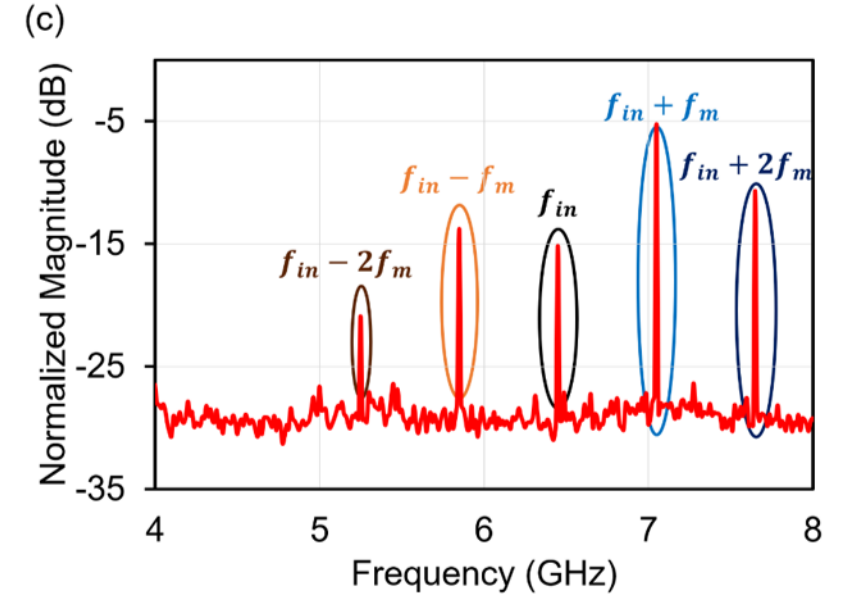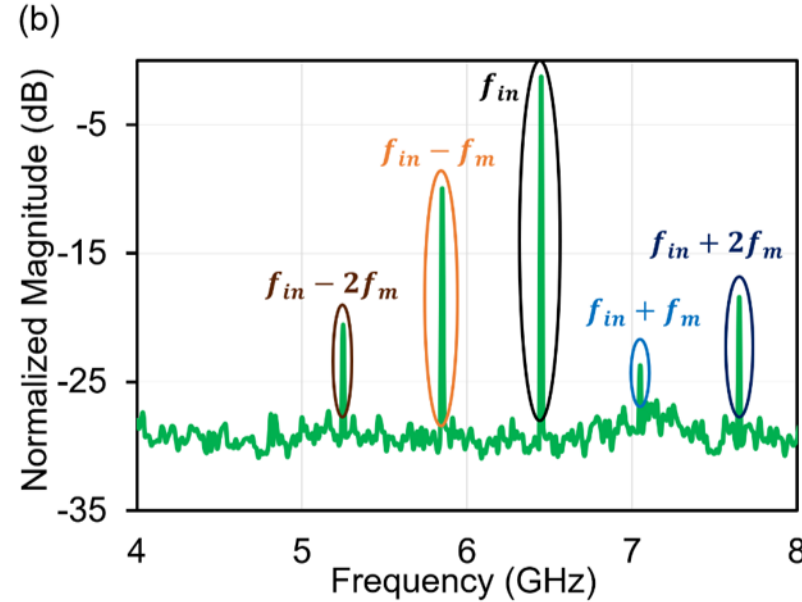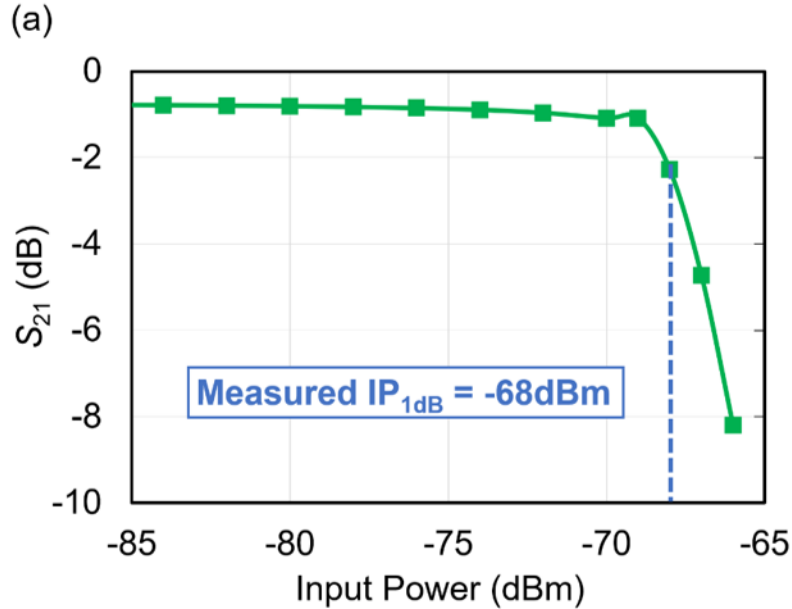- Transmission loss of the filter with no-modulation is 0.27 dB;
- An additional insertion loss of 0.98 dB in the forward direction, isolation is +25 dB at the center frequency and is >15 dB across 250 MHz bandwidth in the reverse direction with modulation.
- Tuning across 6 GHz to 6.75 GHz.



- -1 dB compression point is -68dBm.
- In forward direction, input power concentrated at the input frequency.
- In reverse direction, input power translated to IM frequencies.

- Introduction to Quantum Computing Systems
- Superconducting Non-Reciprocal Bandpass Filter Concept
- Simulation Results
- Measurement Setup and Results
- Conclusion

Conclusion

- Presented a superconducting non-reciprocal BPF that combined BPF and isolator
- Integrated isolators can be 100-1,000× smaller and cheaper compared to ferrite based isolator
- Measured BPF
 - ✓ Insertion loss <1.5dB
 - ✓ Isolation >15dB across 200 MHz
 - ✓ GHz tuning range from 6 GHz to 6.75 GHz